



- Q.4 (a) Design a second order Butterworth high pass filter for cut off frequency of 1 kHz and pass-band gain of  $AF=2$ . [10]  
(b) With a neat circuit derive an expression for the output of an instrumentation amplifier. [10]
- Q.5 (a) With neat circuit explain R/2R ladder digital to analog converter. [10]  
(b) With the help of a functional block diagram explain the working of voltage regulator LM317 to give an output voltage variable from 6 V to 12 V to handle maximum load current of 500 mA. [10]
- Q.6 Short notes on: (Attempt any four)  
(a) Effect of swamping resistor. [05]  
(b) Current fold-back protection circuit in voltage regulator. [05]  
(c) Voltage to Current converter. [05]  
(d) Peak detector circuit. [05]  
(e) Working of PLL IC 565. [05]

\*\*\*\*\*