

22225

21222

3 Hours / 70 Marks

Seat No.

--	--	--	--	--	--	--	--

15 minutes extra for each hour

- Instructions :**
- (1) All Questions are *compulsory*.
 - (2) Answer each next main Question on a new page.
 - (3) Illustrate your answers with neat sketches wherever necessary.
 - (4) Figures to the right indicate full marks.
 - (5) Assume suitable data, if necessary.
 - (6) Use of Non-programmable Electronic Pocket Calculator is permissible.
 - (7) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following :

10

- (a) Draw the symbols of resistor & capacitor. State the unit of measurement of resistance & capacitor.
- (b) Give two points of distinction between half wave & full wave rectifier.
- (c) Define α & β of a transistor.
- (d) Draw the symbols of N channel & P channel JFET.
- (e) Give two points of distinction between active & passive components.
- (f) Give two points of distinction between active & passive transducers.
- (g) State the selection criterion of transducers.

- 2. Attempt any THREE of the following :** **12**
- (a) With suitable graph, define voltage source & current source.
 - (b) Draw a neat diagram of bridge rectifier. Draw input & output waveforms.
 - (c) With suitable diagram, explain the working of P-N junction diode.
 - (d) With suitable diagram, explain the working of NPN transistor.
- 3. Attempt any THREE of the following :** **12**
- (a) Draw the drain & transfer characteristics of JFET.
 - (b) Give the steps followed to measure temperature of metal using given transducer. Draw suitable diagram.
 - (c) List two advantages of Integrated Circuits. Distinguish between analog & digital ICs.
 - (d) With suitable diagram, explain the working of transistor as an amplifier.
- 4. Attempt any THREE of the following :** **12**
- (a) Explain :
 - (i) Seebeck effect
 - (ii) Peltier effect
 - (b) Draw block diagram of regulated power supply. Explain function of each block.
 - (c) With suitable diagram, explain the working of transistor as a switch.
 - (d) A JFET has a drain current of 3 mA. If I_{DSS} is 10 mA & $V_{GS}(\text{OFF})$ is -6V . Find V_{GS} & V_p .
 - (e) With suitable diagram, explain the working of capacitor filter with full wave rectifier. Draw i/p & o/p waveforms.

5. Attempt any TWO of the following :

- (a) (i) From the sinusoidal wave given below, in fig. (i) & fig. (ii) calculate Amplitude, Frequency.

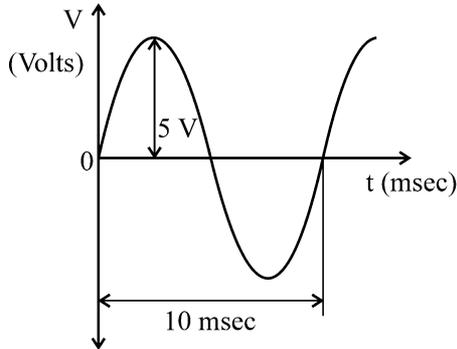


Fig. (i)

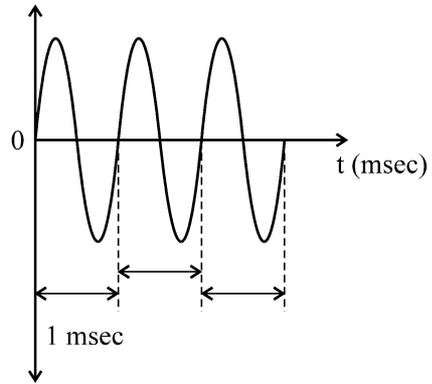


Fig. (ii)

- (ii) Give the value of resistance for the following colour codes –
Red Blue Green Gold.
- (b) (i) In NPN transistor,
 $I_{CE0} = 1000 \mu A$, $\beta = 50$, $I_B = 10 \mu A$
Find I_C & I_E .
- (ii) Define operating point of a transistor.
- (c) (i) Identify the given circuit in fig. (iii) and explain its working.
(ii) Draw the input and output for the same circuit.

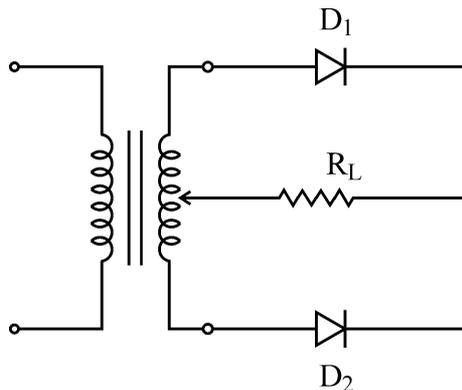


Fig. (iii)

- (iii) State application for the given circuit.

6. Attempt any TWO of the following :**12**

- (a) Draw suitable diagrams showing depletion regions before & after pinch-off for N channel JFET.
 - (b) Distinguish between CB, CC, CE (four points). Explain, why CE configuration is the most preferred combination.
 - (c) With suitable diagram, explain how photodiode & phototransistor can be used as control device for the given application.
-